

Homework 5;

November 22, 2019

Problem 1 (score: 5/10)

- (a) OK
- (b) not ok; function can be realized as

$$(A + B(D + C))(FG + E)$$

12 gates

Problem 2 (score: 5/10)¹

Problem 8 (score: 5/10)²

- (a) NOT ok
- (b) ok

Problem 12 (score: 0/10)³

NOT ok. The first function can be implemented as

$$(b' + d)(a + c + d)(a + b + c)$$

with less gates and inputs as your version. Similar for other functions.

Also, your circuit has more than 9 gates.

Problem 42 (score: 0/10)⁴

¹similar problems: ff

enumerate[(a)]

NOT ok. The function can be implemented as

$$a'bc + a'bd' + ab'c' + ab'd'$$

this has the same number of gates, but less inputs than your version

ok ²similar problems:

³similar problems:

⁴similar problems: